

Which resistive component is designed to be temperature sensitive?

- A. Thermistor
- B. Rheostat
- C. Potentiometer
- D. Photoconductive cell

**Answer:** Option A

---


2. Batteries differ from fuel cells in that

- A. a battery is a closed system
- B. a battery uses hydrogen and oxygen to create electricity
- C. a battery uses a polymer electrolyte membrane
- D. none of the above

**Answer:** Option A

---

3.

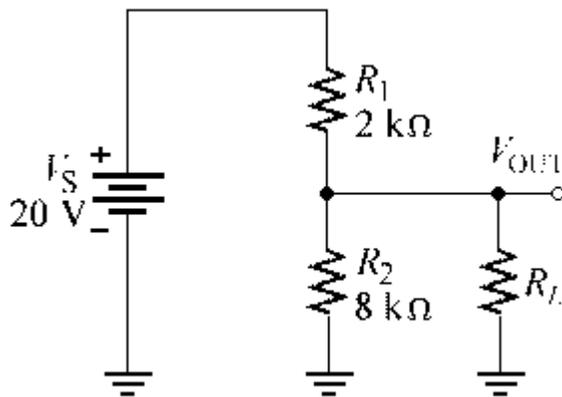

If the load in the given circuit is  $120\text{ k}\Omega$ , what is the loaded output voltage?

- A. 4.21 V
- B. 15.79 V
- C. 16 V
- D. 19.67 V

**Answer:** Option B

---

4. The \_\_\_ of a capacitor affects the time it takes to charge and discharge.

- A. package style
- B. lead arrangement
- C. plate area
- D. voltage rating

**Answer:** Option C

5. The secondary current in a transformer depends on the secondary voltage and load resistance values.

- A. True
- B. False


**Answer:** Option A

6. If a  $7.5\text{ k}\Omega$  resistance is connected to a  $10\text{ k}\Omega$  inductive reactance in a series  $RL$  circuit, then the impedance equals  $12.5\text{ k}\Omega$ .

- A. True
- B. False

**Answer:** Option A

7.

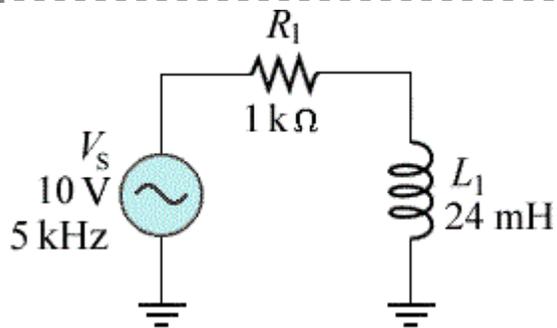


The voltage dropped across the resistor in the circuit in the given circuit is approximately equal to \_\_\_.

- A. 5 V
- B. 10 V
- C. 7.98 V
- D. 6.02 V

**Answer:** Option C

8.

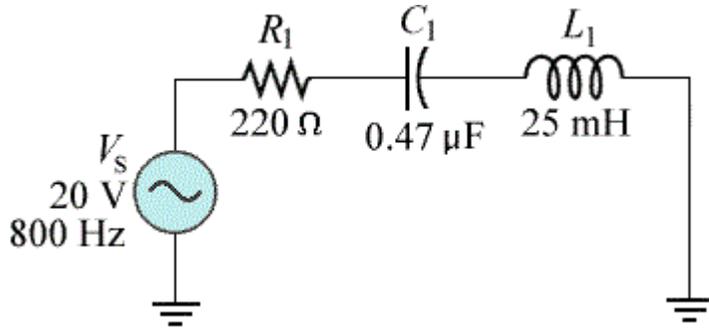

What is the impedance of the circuit in the given circuit?

- A.  $125.7 \Omega$
- B.  $297.6 \Omega$
- C.  $370.1 \Omega$
- D.  $423.3 \Omega$

**Answer:** Option C

9. If a periodic pulse waveform is applied to an RC differentiating circuit, which two conditions are possible?

- A.  $t_w \geq 5 \tau$  or  $t_w > 5 \tau$
- B.  $t_w = 5 \tau$  or  $t_w > 5 \tau$
- C.  $t_w \leq 5 \tau$  or  $t_w < 5 \tau$
- D.  $t_w \geq 5 \tau$  or  $t_w < 5 \tau$

**Answer:** Option D

10. A pn junction allows current flow when

- A. the p-type material is more positive than the n-type material
- B. the n-type material is more positive than the p-type material
- C. both the n-type and p-type materials have the same potential
- D. there is no potential on the n-type or p-type materials

**Answer:** Option A

11. The voltage produced by a thermocouple is called the \_\_\_\_\_.

- A. hot junction voltage
- B. cold junction voltage
- C. Seebeck voltage
- D. Hooke voltage

**Answer:** Option C

---

12. The six basic forms of energy are:

- A. light, sun, magnetic, chemical, electrical, and mechanical
- B. electrical, mechanical, light, heat, magnetic, and chemical
- C. electrical, mechanical, sun, heat, chemical, and light
- D. potential, sun, light, chemical, electrical, and mechanical

**Answer:** Option B

---

13. If the frequency of a radio wave is increased, then its wavelength will:

- A. increase
- B. decrease
- C. remain the same
- D. cannot tell

**Answer:** Option B

---

14. A bipolar junction transistor has \_\_\_\_\_ regions of operation.

- A. 1
- B. 2
- C. 3
- D. 4

**Answer:** Option B

---

15. A NAND gate consists of an AND gate and an OR gate connected in series with each other.

- A. True
- B. False

**Answer:** Option B

---

16. Which of the following summarizes the important features of emitter-coupled logic (ECL)?

---

- A. negative voltage operation, high speed, and high power consumption
- B. good noise immunity, negative logic, high frequency capability, low power dissipation, and short propagation time
- C. slow propagation time, high frequency response, low power consumption, and high output voltage swings
- D. poor noise immunity, positive supply voltage operation, good low-frequency operation, and low power

**Answer:** Option A

---

17. A multiplexed display circuit uses a technique called time division modulation.

- A. True
- B. False

**Answer:** Option B

---

18. Memory configuration refers to the organization of storage bits within a memory.

- A. True
- B. False

**Answer:** Option A

---

19. The difference between analog voltage represented by two adjacent digital codes, or the analog step size, is the:

- A. quantization
- B. accuracy
- C. resolution
- D. monotonicity

**Answer:** Option C

---

20. A machine cycle is the time it takes a microprocessor to fetch and execute a complete instruction.

- A. True
- B. False

**Answer:** Option B

---